

ELEKTRIJADA 2010 – Power System Analysis

ANNOTATION: You must chose only one of given answers for problems. Right answers worth given number of points. Wrong answers worth -25 % of given points. For answer “I don’t know” there are no negative points.

1. (5 points) Official unit for reactive power is:

- a) VAr
- b) VAR
- c) var
- d) No one of given answers
- e) I don’t now

2. (5 points) Lossless transmission line ($r=0, g=0$) with no load at one end is given. Voltages at ends of line are $\underline{U}_1 = U_1 e^{j\delta_1}$ and $\underline{U}_2 = U_2 e^{j\delta_2}$. One of following statement is true. The answer is:

- a) $U_1 = U_2, \delta_1 = \delta_2$
- b) $U_1 \neq U_2, \delta_1 = \delta_2$
- c) $U_1 = U_2, \delta_1 \neq \delta_2$
- d) No one of given answers
- e) I don’t now

3. (8 points) Transmission line ($U_n = 220$ kV, $f_n = 50$ Hz) with parameters:

$$r_v = 0,125 \Omega/\text{km}; \quad x_v = 0,4 \Omega/\text{km};$$


$$g_v = 0,1 \cdot 10^{-6} \text{ S}/\text{km}; \quad c_v = 9 \cdot 10^{-9} \text{ F}/\text{km};$$

$$L_v = 100 \text{ km},$$

is given. Find characteristic impedance for transmission line. The answer is:

- a) $\underline{Z}_c = 384,87 e^{j7,66^\circ} \Omega$
- b) $\underline{Z}_c = 356,9 e^{-j5,86^\circ} \Omega$
- c) $\underline{Z}_c = (381,43 - j51,33) \Omega$
- d) No one of given answers
- e) I don’t now

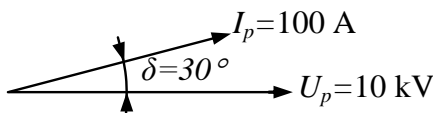4. (8 points) Voltage and current phasor diagram of one single phase consumer is shown on the figure. Find consumer power.




The answer is:

- a) $\underline{S}_p = (500\sqrt{3} + j500) \text{ kVA}$
- b) $\underline{S}_p = (1000 - j500\sqrt{3}) \text{ kVA}$
- c) $\underline{S}_p = 1000 e^{j30^\circ} \text{ kVA}$

- d) No one of given answers
- e) I don’t now

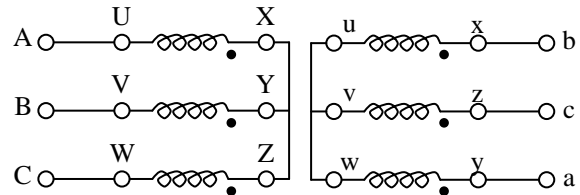5. (10 points) For transformer, given at the figure, find vector group.




The answer is:

- a) 2
- b) 8
- c) 10
- d) No one of given answers
- e) I don’t now

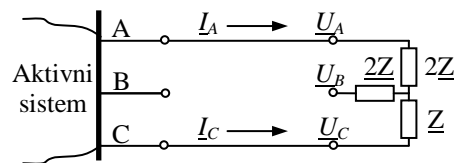6. (10 points) Active network supply nonsymmetrical consumption (see figure).

There are known: $\underline{I}_A = 2 e^{j60^\circ} \text{ p.u.}$, $\underline{I}_C = 2 e^{-j120^\circ} \text{ p.u.}$, $\underline{U}_B = \sqrt{3} \text{ p.u.}$ and $\underline{Z} = 1,5 e^{j30^\circ} \text{ p.u.}$ Find consumer voltage zero sequence component.




The answer is:

- a) $\underline{U}_o = (3\sqrt{3} + j3) \text{ p.u.}$
- b) $\underline{U}_o = 2 e^{j30^\circ} \text{ p.u.}$
- c) $\underline{U}_o = (\sqrt{3}/3 + j1) \text{ p.u.}$
- d) No one of given answers
- e) I don’t now

7. (12 points) At the end of transmission line, with parameters $R=0,02$ p.u., $X=0,08$ p.u., $B=0,16$ p.u., is connected passive consumption area. Voltage magnitude at the beginning and the end of line are $U_1=1.1$ p.u. i $U_2=1$ p.u. respectively. Phase difference between voltage phasors is $\delta=9^\circ$. Find active and reactive power of consumption area. The answer is:

- $\underline{S}_p = (2,28 + j0.51)$ p.u.
- $\underline{S}_p = (2,28 + j0.43)$ p.u.
- $\underline{S}_p = (2,28 + j0.59)$ p.u.
- No one of given answers
- I don't now

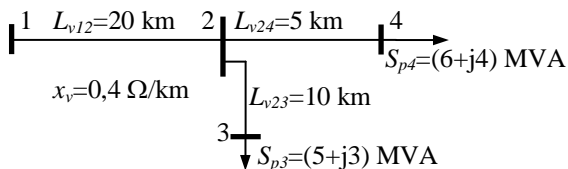
8. (12 points) Radial network is given on the figure.



With shunt capacitor bank on the buses 3 and 4 with same reactive power, voltage magnitudes at buses 3 and 4 are $U_3=U_4=10$ kV. Find that reactive power of shunt capacitor bank. The answer is:

- $\underline{S}_{BK} = jQ_{BK} = j1,95$ MVA
- $\underline{S}_{BK} = jQ_{BK} = j2,63$ MVA
- $\underline{S}_{BK} = jQ_{BK} = j2,32$ MVA
- No one of given answers
- I don't now

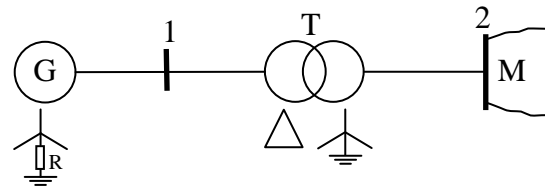9. (15 points) Simply power system with data is shown on the figure.




G: $S_{nG}=50$ MVA, $U_{nG}=10$ kV,
 $x'_{dg}=x_{ig}=30\%$, $x_{og}=10\%$
T: $S_{nT}=S_{nG}$, $m_T=220/10$ kV/kV, $x_T=10\%$
M: Strong network with “ ∞ ” power.

Find value of resistance R which limits single phase to ground current at bus 1 at value 1000 A. Voltage at bus 1 before fault was equal to generator nominal voltage. The answer is:

- $R=5,77 \Omega$
- $R=10 \Omega$
- $R=17,31 \Omega$
- No one of given answers
- I don't now

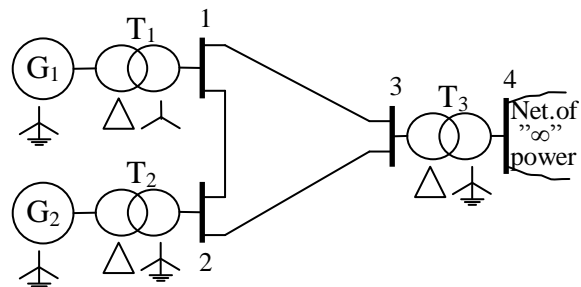10. (15 points) Simply power system is shown on the figure. System data are given in the table.



	G_1	G_2	T_1	T_2	T_3	Lines
X_d (p.u.)	0.14	0.14	0.06	0.06	0.05	0.1
X_i (p.u.)	0.14	0.14	0.06	0.06	0.05	0.1
X_o (p.u.)	0.05	0.05	0.06	0.06	0.05	0.3

In the case of single phase to ground fault of phase A at bus 3, find phase A current for transformer T_2 . Voltage at bus 3 before fault was $U_{3fr}=1$ p.u. The answer is:

- $\underline{I}_{AT2} = -j2,941$ p.u.
- $\underline{I}_{AT2} = -j3,731$ p.u.
- $\underline{I}_{AT2} = -j3,517$ p.u.
- No one of given answers
- I don't now